

CSE 260M / ESE 260

Intro. To Digital Logic & Computer Design


Bill Siever
&
Jim Feher

This week

- Thursday:
Studio — Here / Seigle 301
- Midterm Grades: Canvas
 - Studios and Pre-lecture grades posted
 - Hw 1-4 returned / grades posted
 - Exam 1 returned / grades posted


Exam

Dff: Setup & Hold Time

 


Dff Time Parameters

 - t_{pcq} : Propagation delay from Clock to Q (pcq)
- t_{ccq} : Contamination delay from Clock to Q (ccq)




Moore Machine: How fast can it go?

 


Fastest Clock Rate?

 - R2's input needs to be stable t_{setup} before clock
- Variation of Moore Machine:
Imagine no R2 - a loop to R1
- $T_c \geq t_{pcq} + t_{pd} + t_{setup}$




Hold Time Constraint

 - Min time from R1 through CL
 - R2's input must be stable t_{hold} after the clock



Hold Time Constraint

- Min time from R1 through CL
 - R2's input must be stable t_{hold} after the clock
 - Both t_{ccq} and t_{hold} are provided/set
- $t_{cd} \geq t_{hold} - t_{ccq}$
May need to add delays in Combo. Logic to meet

 

Chapter 4

HDL

- HDL is a way to *describe* hardware
- HDLs typically can describe hardware in different ways
- HDLs describe hardware in modules

HDLs *Describe* Hardware

- Uses
 - Simulation: Confirm modules work together
 - “Synthesis” : Transformation to real hardware
 - Like compilers used for programming languages
- Description Styles
 - Structure (connect 2 input AND to ...)
 - Behavior (if x then y)


HDL

- A HDL is not a computer program.
- A HDL is not a computer program!
- A HDL is *not* a computer program!
- A HDL is not a computer program!
- A HDL is ***NOT*** a computer program!


We will use Verilog

Not VHDL

(System) Verilog Module Example

 


(System) Verilog Module Example

 


```
module example(input logic a, b, c,  
                output logic y);  
    // module body goes here  
endmodule
```

 Input & Output
are like the Pins
On chips or in
JLS




HDL: *Structural* (Verilog)
 
```
module nand3(input logic a, b, c  
              output logic y);  
    logic n1;           // internal signal  
  
    and3 andgate(a, b, c, n1); // instance of and3  
    inv inverter(n1, y);     // instance of inv  
endmodule
```




HDL: *Structural* (Verilog)

 

```
module nand3(input logic a, b, c
              output logic y);
    logic n1;           // internal signal
    inv inverter(n1, y); // instance of inv
    and3 andgate(a, b, c, n1); // instance of and3
endmodule
```

HDL: *Behavioral* (Verilog)

 
```
module nand3(input logic a, b, c  
              output logic y);  
    assign y = ~(a & b & c);  
endmodule
```



4-bit mux2: Behavior


- Conditionals via Ternary operator (? :)
- Multi-bit values via [] notation
 
```
module mux2 (input logic [3:0] d0,  
              input logic         s,  
              output logic [3:0] y);  
    assign y = s ? d1 : d0;  
endmodule
```



8-bit mux2: Hierarchical
 
```
module mux2_8(input logic [7:0] d0, d1,  
               input logic      s,  
               output logic [7:0] y);  
  
    mux2 lsbmux(d0[3:0], d1[3:0], s, y[3:0]);  
    mux2 msbmux(d0[7:4], d1[7:4], s, y[7:4]);  
endmodule
```



Sequential Logic

always: Based on *Events*

- Concept of “event” is related to simulation and “event driven programming”
- JLS uses events: An OR gate “reacts” to events and schedules an update
See here


always Statement

- **Form:**

```
always @(sensitivity list)
    statement;
```


- **When event in sensitivity list occurs, statement is executed**

Verilog: D Flip-Flop

 

```
module flop(input logic clk,  
           input logic [3:0] d,  
           output logic [3:0] q);  
    always_ff @(posedge clk)  
        q <= d; // pronounced "q gets d"  
endmodule
```


Resettable D-Flip-Flop 1

 

```
module flopr(input logic clk,
              input logic reset,
              input logic [3:0] d,
              output logic [3:0] q);

  always_ff @ (posedge clk)
    if (reset) q <= 4'b0;
    else       q <= d;
endmodule
```


Resettable D-Flip-Flop 2

 

```
module flopr(input logic      clk,
              input logic      reset,
              input logic [3:0] d,
              output logic [3:0] q);

  always_ff @ (posedge clk, posedge reset)
    if (reset) q <= 4'b0;
    else        q <= d;
endmodule
```

Resettable D-Flip-Flop 3

 

```
module flopr(input logic clk,
              input logic reset,
              input logic en,
              input logic [3:0] d,
              output logic [3:0] q);

    always_ff @ (posedge clk, posedge reset)
        if (reset)      q <= 4'b0;
        else if (en)    q <= d;
endmodule
```

always and Combinational Logic

Block of
assignments

```
always_comb
begin
    y = a & b
    ...
end
```

Could have
been done with
individual assigns

Notice = (“blocking assignment”),
not <= (“non-blocking assignment”)

always_comb has nice features

- **case** : Selection between several options
Great for state machines!
 - Must describe all possible combinations to be comb logic. Use default

```
case (state)
    soap:           hot = 1;
    highPressureWarm: hot = 1;
    ...
    default: hot = 0;
endcase
```

Questions

- Will we use a HDL? Yes
- [Which HDL?]: Verilog
- Test benches?
- Is my degree worth it? (I think mine was. Your mileage may vary...)

Next Time

- Studio